

# OPAMP

## Lecture 14

Manoj Kr. Das  
Associate Professor  
Physics Department  
J N College, Boko

## OPAMP as Scale Changer:

As shown in *Fig 1*, non-inverting terminal is grounded and virtual short circuit exist at input terminal. Here  $R_1 = R_f$ . The output voltage  $V_0$  is equal to  $(-V_1)$  i.e. slightly sign of the input voltage changed. Hence such a circuit is known as a phase inverting amplifier and is called sign or scale changer.

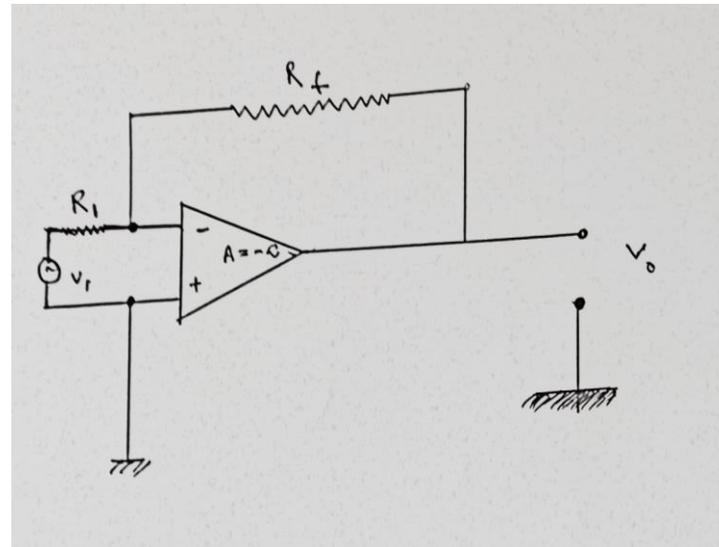


Fig 1

In case inverting amplifier, let  $\frac{R_1}{R_f} = K$ , where  $K$  is real constant, then output voltage

$$V_o = -KV_1 \rightarrow (i)$$

Thus output voltage scale is obtained by multiplying input voltage scale  $-k$ , called Scale Factor. Then inverting amplifier can be served as a scale changer. A low voltage can be accurately measured by amplifying a voltage by a scale changer and dividing the amplified voltage by scale factor.

## Adder or Summing Amplifier:

As shown in *Fig 2* as  $G$  is virtual ground i.e. at ground potential, the input impedance is infinite, the current  $i_1, i_2, \dots, i_n$  be equal to  $i_0$  i.e.

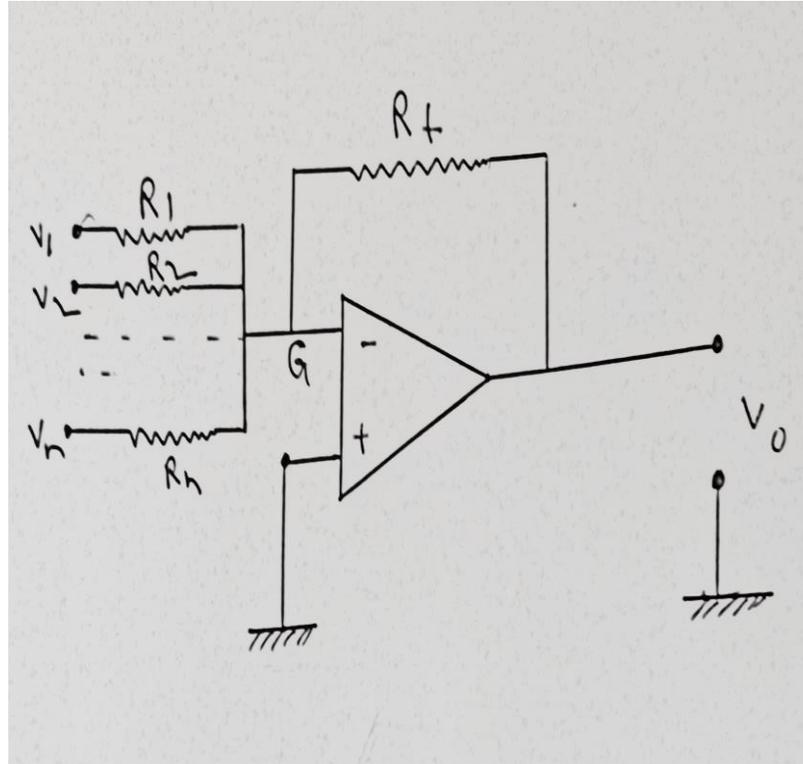


Fig 2

$$i_1 + i_2 + \dots + i_n = i_0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} = -\frac{V_0}{R_f}$$

$$V_0 = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \dots + \frac{R_f}{R_n}V_n\right)$$

If

$$R_1 = R_2 = \dots = R_n = R$$

Then

$$V_0 = -\frac{R_f}{R}(V_1 + V_2 + \dots + V_n)$$

If

$$R_f = R$$

Then

$$V_0 = -(V_1 + V_2 + \dots + V_n) \rightarrow (ii)$$

This shows that output  $V_0$  is numerically equal to algebraic summation of input voltage  $V_1, V_2, \dots, V_n$ .

Then

$$V_0 = -\frac{R_f}{R} (V_1 + V_2 + \dots + V_n) \rightarrow (iii)$$

So the circuit is known as Summing Amplifier or Adder. If algebraic sum of input voltage is small, the output voltage  $V_0$  is measured with  $R_f > R$

## Differential Amplifier or Subtractor:

Let as shown in *Fig 3* difference between  $V_2$  and  $V_1$  is to be amplified. The voltage gain of OPAMP be infinite and point A and B will have same potential say  $V_x$ , then we can write

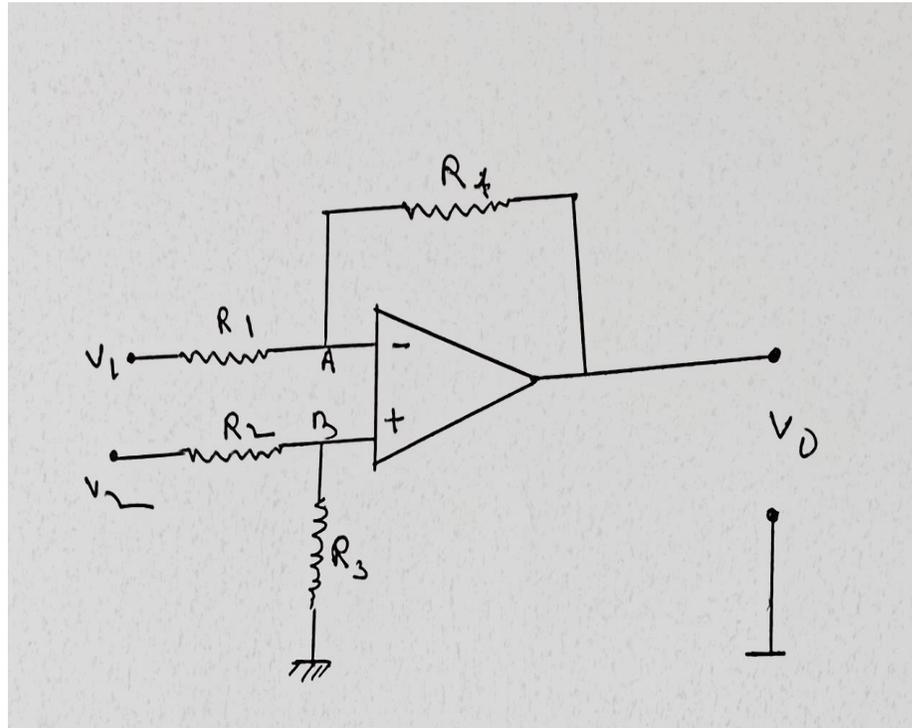


Fig 3

$$\frac{V_1 - V_x}{R_1} = \frac{V_x - V_0}{R_2}$$

$$\frac{V_2 - V_x}{R_1} = \frac{V_x}{R_2}$$

Where we have assumed that the input impedance of OPAMP is infinite. Subtracting the two equations we get

$$V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

Where  $V_0$  is amplified version of difference  $(V_2 - V_1)$ . The voltage gain of amplifier system being  $\frac{R_2}{R_1}$ . If  $R_1 = R_2$ , the circuit serve as subtractor, the output voltage gain the difference of  $(V_2 - V_1)$ .

### **Differentiator:**

This circuit as shown in *Fig 4* gives the output voltage  $V_0$ , which is proportional to the derivative of input voltage  $V_1$  with respect to time. The infinite voltage gain of OPAMP makes G, a virtual ground. The charge of capacitor  $C$  is

$$q = CV_1$$

$$V_1 = \frac{q}{C}$$

Where  $i$  is current flows through capacitor  $C$  . Since input impedance of OPAMP is infinite the current  $i$  flows through resistance  $R$ . Therefore

$$i = -\frac{V_0}{R}$$

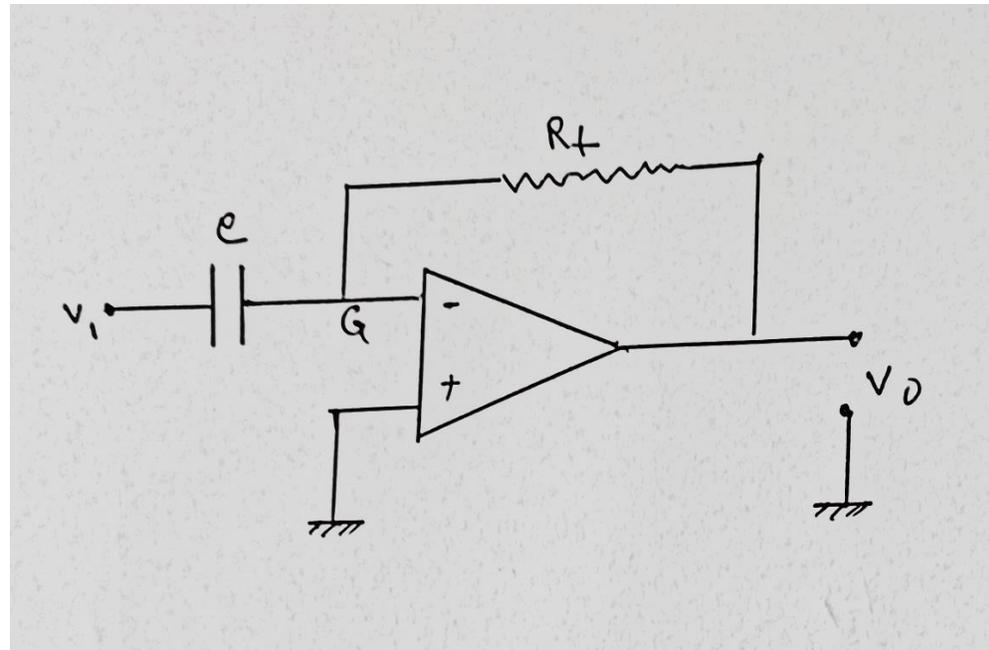


Fig 4

Therefore

$$V_0 = -CR \frac{dV_1}{dt}$$

Obviously output voltage of  $V_0$  is proportional to the time derivative of input voltage  $V_1$ , the proportionality constant is  $(-CR)$ .

### **Integrator:**

As shown in Fig 5, the point G is again at virtually grounded and the gain is infinite. The current flowing through resistance  $R$  is

$$i = \frac{V_1}{R}$$

The input impedance of OPAMP being infinite the current  $i$  flows through a feedback capacitance  $C$  to produce output voltage  $V_0$ .

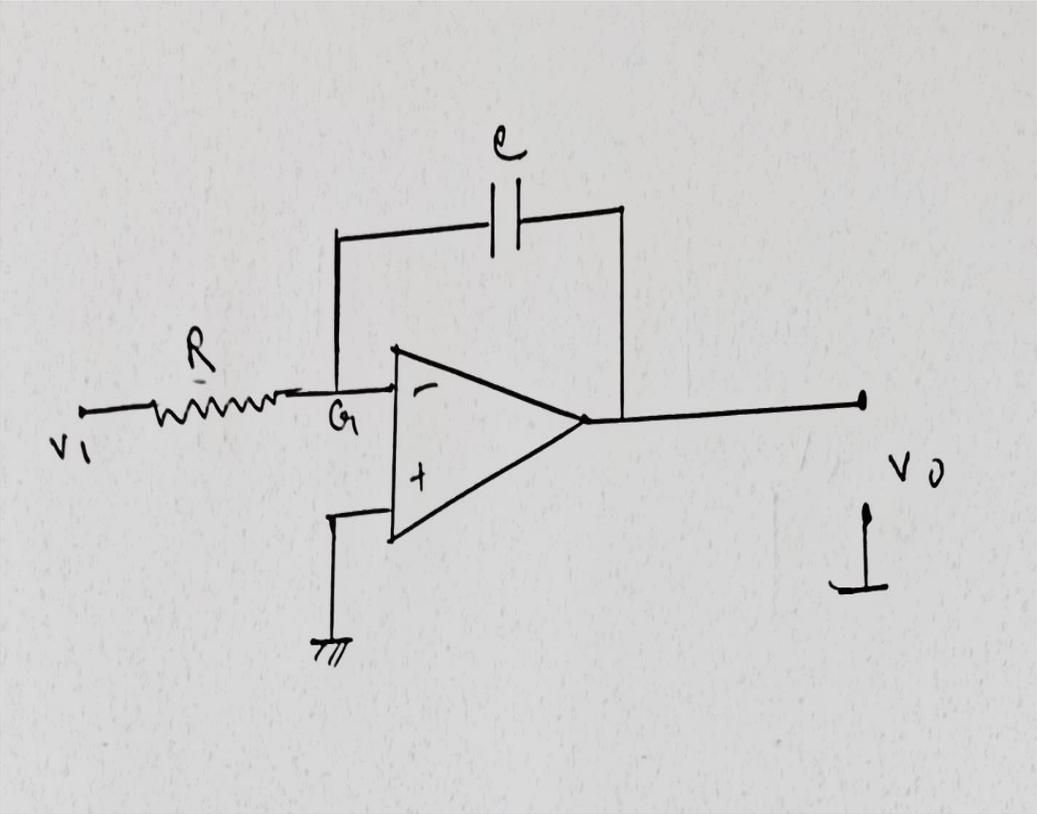


Fig 5

Therefore

$$V_0 = -\frac{1}{C} \int_0^t i dt$$

$$V_0 = -\frac{1}{CR} \int_0^t V_1 dt$$

The output voltage  $V_0$  is thus proportional to time integral of input voltage  $V_1$ , the constant of proportionality is  $\left(-\frac{1}{CR}\right)$ .